

Determining capacitor size and maximum sampling frequency for a nRF51 ADC voltage divider

The nRF51 ADC voltage divider model

The voltage divider circuit is as shown in figure 1.

 


Figure 1. Voltage divider circuit for the nRF51 ADC

t_{SAMPLE} – 8 bit resolution	20 μs
t_{SAMPLE} – 9 bit resolution	36 μs
t_{SAMPLE} – 10 bit resolution	68 μs
R_{AIN} – 1/1 prescale	129.7 k Ω
R_{AIN} – 2/3 prescale	194.6 k Ω
R_{AIN} – 1/3 prescale	389.2 k Ω
U_{ADC} – VBG reference	0.6 V
1 bit voltage for 8 bit resolution	4.71 mV
1 bit voltage for 9 bit resolution	2.35 mV
1 bit voltage for 10 bit resolution	1.17 mV

Table 1. nRF51 ADC values

Before ADC sampling, the capacitor C will charge up since the input to the ADC is high impedance, i.e. $R_{AIN} = \infty$. When the ADC samples, R_{AIN} will have value as shown in table 1. Duration of each sample is t_{SAMPLE} , also shown in table 1.

When sampling, current will flow from capacitor C into the ADC through resistor R_{AIN} . The charge of the capacitor will hold U_{AIN} steady during the sampling period, therefore eliminating the error caused by the high impedance voltage divider. The capacitor will of course discharge a little when sampling but the capacitor needs to be dimensioned so that the voltage error is less than what corresponds to 1 bit.

Deriving general equations

Steady state voltages for the circuit in Figure 1 are:

$$U_{AIN_SS_sampling} = U_{BATT} * \frac{R_2 || R_{AIN}}{R_2 || R_{AIN} + R_1} + U_{ADC} * \frac{R_1 || R_2}{R_1 || R_2 + R_{AIN}}$$

$$U_{AIN_SS_not_sampling} = U_{BATT} * \frac{R_2}{R_1 + R_2}$$

where:

$$R_1 || R_2 = \frac{R_1 * R_2}{R_1 + R_2}$$

The discharge voltage for the capacitor in Figure 1 is:

$$U_{C_discharge} = U_0(e^{-t/RC})$$

Setting the discharge boundary equal to 1 bit voltage gives:

$$U_0 - U_{1bit} = U_0(e^{-t/RC})$$

Isolating for C gives

$$C = \frac{-t}{R * \ln\left(\frac{U_0 - U_{1bit}}{U_0}\right)} \quad (\text{equation 1})$$

where:

$$U_0 = U_{AIN_SS_not_sampling} - U_{AIN_SS_sampling}$$

$$t = t_{SAMPLE}$$

$$R = R_2 || R_{AIN} || R_1$$

$$U_{1bit} = 1 \text{ bit voltage}$$

Finding the maximum sampling frequency

Capacitor charging equation is

$$U_{C_charge} = U_0(1 - e^{-t/RC})$$

The capacitor is estimated to be fully charged after $5*RC$ (99.3%). Maximum sampling frequency is therefore $f_{max} = \frac{1}{5*RC}$

where:

$$R = R_2 || R_1$$

Calculation example

For the example, following values are selected:

$$U_{BATT} = 4.2V$$

$$R_1 = 10M\Omega$$

$$R_2 = 2.2M\Omega$$

ADC prescaler: 1/1 ($R_{AIN} = 129.7k\Omega$)

ADC resolution: 10 bit (68 μ s sampling period)

To find the capacitor value we insert the selected values into equation 1:

$$U_{AIN_SS_sampling} = 4.2 * \frac{2.2M || 129.7k}{2.2M || 129.7k + 10M} + 0.6 * \frac{10M || 2.2M}{10M || 2.2M + 129.7k} = 0.0508 + 0.5597 = 0.6106 V$$

$$U_{AIN_SS_not_sampling} = 4.2 * \frac{2.2M}{2.2M + 10M} = 0.7574 V$$

$$U_0 = U_{AIN_SS_not_sampling} - U_{AIN_SS_sampling} = 0.7574 - 0.6106 = 0.1468 V$$

$$t = t_{SAMPLE} - 10 \text{ bit resolution} = 68 \mu s$$

$$R = R_2 || R_{AIN} || R_1 = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_{AIN}} \right)^{-1} = \left(\frac{1}{10M} + \frac{1}{2.2M} + \frac{1}{129.7k} \right)^{-1} = 121.0 k\Omega$$

$$U_{1bit} = 1 \text{ bit voltage for 10 bit resolution} = 1.17 mV$$

$$C = \frac{-68\mu}{121.0k * \ln\left(\frac{146.8m - 1.17m}{146.8m}\right)} = 70.3 nF$$

The maximum sampling frequency for this setup is:

$$f_{max} = \frac{1}{5 * RC} = \frac{1}{5 * R_2 || R_1 * C} = \frac{1}{5 * 1.803M * 70.3n} = 1.58 Hz$$